

Evan Smith


Quiz 3

Problem 1:

1. Wire delay using the lumped RC Model: $0.69 * R_{\text{driver}} * 1\text{pF} = 0.69 * R_{\text{driver}}$ ps, not sure if the wire resistance counts as driver here. If so, this gives **34.5μs**. If not, this would be assumed to have **no delay at all**, since the 0Ω driver resistance makes the time disappear.
2. Wire delay using the Distributed RC Model:
 $0.38 * R * C = 0.38 * 0.05(1\text{cm}/1\mu\text{m}) * 1\text{pF}$
 $= 0.38 * 50\text{K}\Omega * 1\text{pF} = 19\mu\text{s}$

Problem 2:

Parts A and B below:

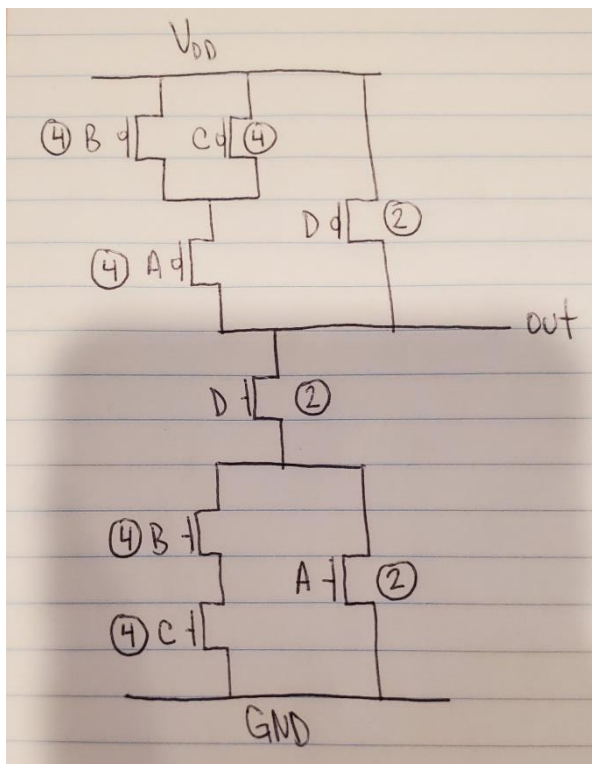

C: **Worst Pull-Up Input: [ABCD] 0101**

Worst Pull-Down Input: [ABCD] 0111

D: **Worst tpHL would be moving between the states from Part C -> 0101 to 0111**